

Index

Sl No.	Name of the Experiment	Page No.	Date of Experiment	Date of Submission	Remarks
1.	Measure unknown inductance following bridge (a) Maxwell bridge.	01 to 03			
2.	Measure low resistance by Kelvin's double bridge.	04 to 06			
3.	Calibrate an ammeter using DC slide wire potentiometer.	07 to 10			
4.	Measure low resistance by Crompton potentiometer.	11 to 13			
5.	Measurement of displacement with the help of LVDT.	14 to 17			

Experiment :- 1

» AIM:-

To measure the maxwell bridge.

- (i) Inductance of a coil
- (ii) Q factor of the coil using Maxwell's bridge.

» APPARATUS:-

S.No.	apparatus	Range	Quantity
1	Maxwell bridge kit	-	1
2	Inductive coil	-	1
3	Headphone	-	1

» THEORY:-

In the bridge an inductance is measured by comparison with a standard variable capacitance.

Under balanced condition

$$(R_1 + j\omega L_1) \left[\frac{R_4}{1 + j\omega C_4 R_4} \right] = R_2 R_3$$

$$R_1 R_4 + j\omega R_1 R_4 = R_2 R_3 + j\omega R_2 R_3 C_4 R_4$$

Comparing the real and imaginary parts.

$$R_1 = \frac{R_2 R_3}{R_4} \quad \text{and} \quad L_1 = R_2 R_3 C_4$$

The expression for Q factor of the coil is $Q = \frac{\omega L_1}{R_1} = \omega C_4 R_4$

» PROCEDURE:-

- Connection to be made as per the circuit diagram.
- The balance condition is obtained by adjusting capacitance.
- The balance condition is checked with a help of headphones.
- All the value in the bridge are noted down.

L_1 = Unknown inductance

R_1 = effective resistance of inductor

C_4 = variable standard capacitor


$R_2 R_3 R_4$ = known non-inductive resistance.

* Tabulation:-

» Maxwell bridge method.

S.R Num	Given Inductance	Capacitance	Resistance	Resi.....	L=PRC
Unit	Henry	μF	k Ω (R_m)	k Ω (R_2)	mH
1	600	0.6	1000	1000	600
2	520	0.5	1000	1000	500
3	550	0.6	1000	1000	600

Teacher's Signature: _____

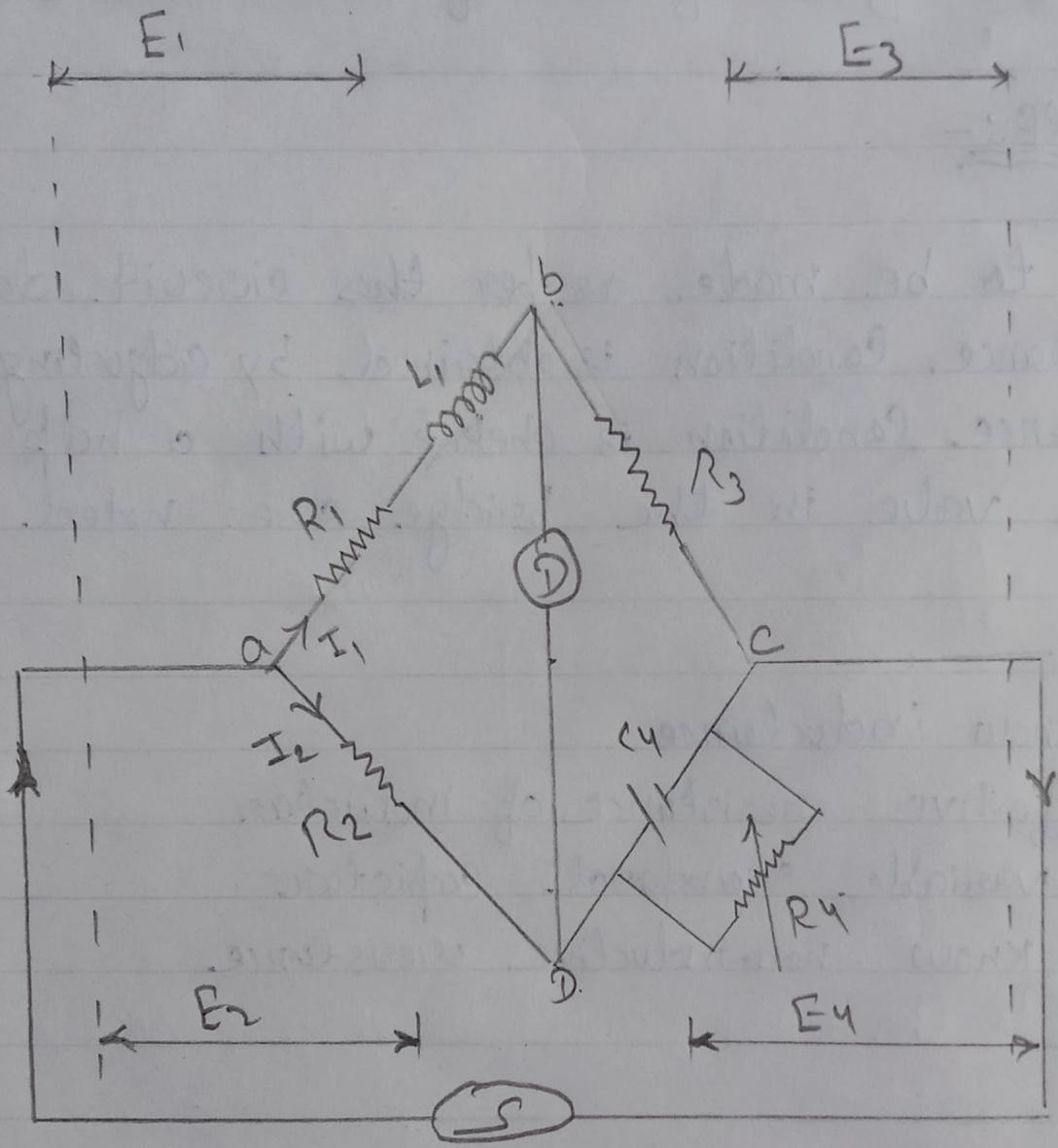

MAXWELL'S INDUCTANCE CAPACITANCE BRIDGE

Sl. No.	Frequency (Hz)	Inductance (mH)	Capacitance (μF)	Resistance (Ω)	Galvanometer Deflection
1	1000	100	100	100	0
2	1000	200	200	200	0
3	1000	300	300	300	0
4	1000	400	400	400	0
5	1000	500	500	500	0

>> MODEL Calculation

$$P = 1000 \Omega$$

$$R = 1000 \Omega$$

$$C = 0.655 \times 10^{-6} \text{ mf}$$

$$L = PRC$$

$$= 1000 \times 1000 \times 0.6 \times 10^{-6}$$

$$= 0.6$$

$$= 600 \text{ mH}$$

>> RESULT:-

Thus the inductance of the given coil is found by Maxwell bridge.

Experiment :- 02

» AIM:-

To measure unknown value of low resistance by balancing the Kelvin's double bridge.


» APPARATUS REQUIRED

S.No	Apparatus	Range	Quantity
1	Kelvin's double bridge	-	1
2.	Galvanometer	-	1
3.	Patch cords	-	3
4.	Unknown resistance	-	1

» THEORY:- It is modification of wheatstone bridge. In the fig. P and Q are the first set of ratio arms. P and Q are the second set of ratio use connected the Galvanometer. The ratio $\frac{P}{Q}$ is made equal to $\frac{p}{q}$. Under balanced conditions there is no current through the galvanometer.

$$E_{ab} = E_{acd}$$
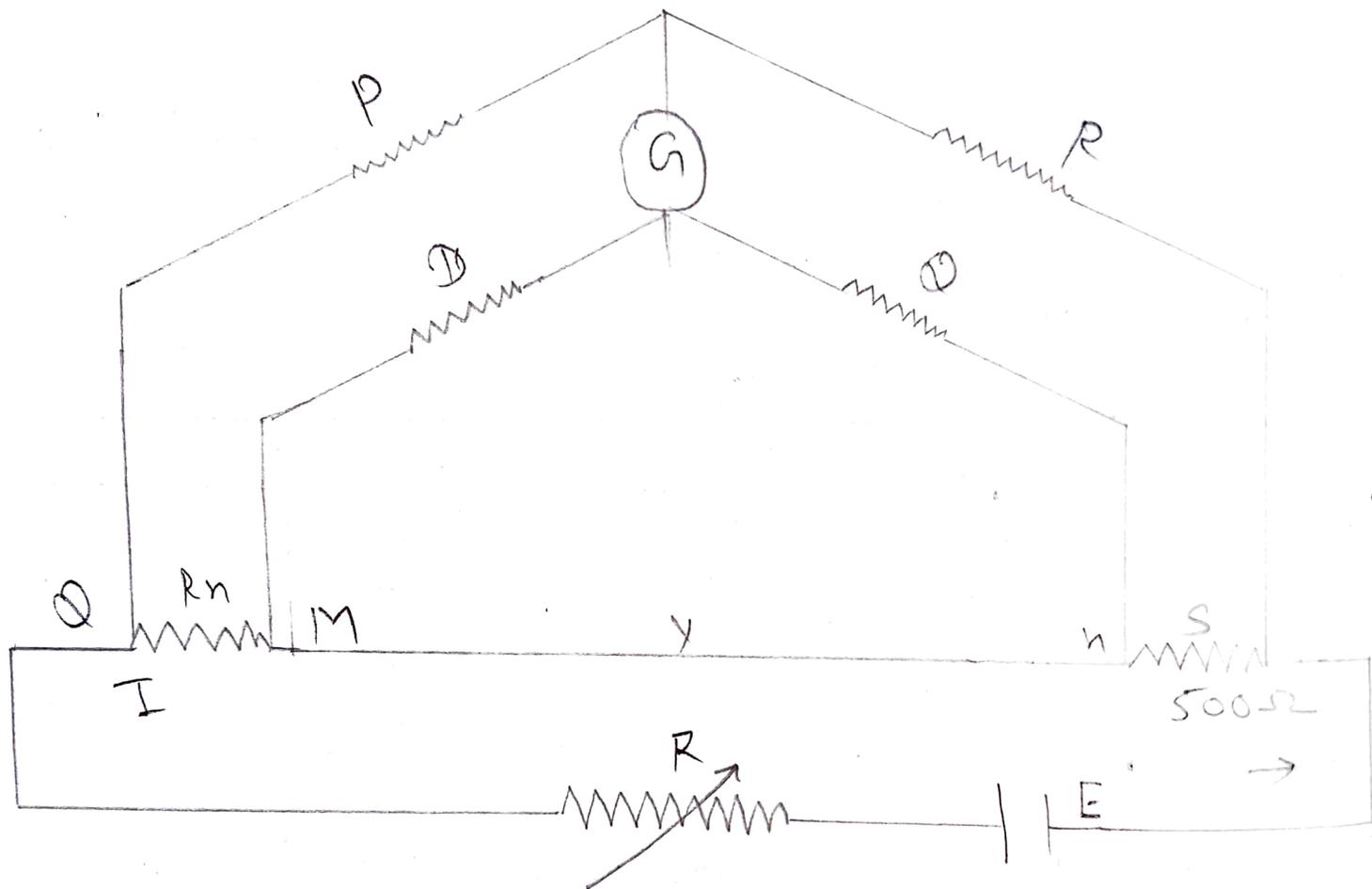
$$E_{ab} = \frac{P}{P+Q} E_{ac} \text{ and}$$



KELVIN'S DOUBLE BRIDGE

$$E_{ac} = \left[IR_n + S + \frac{(P+q)r}{(P+q+r)} \right]$$

and

$$E_{ad} = \left[IR_n + \frac{Pr}{(P+q+r)} \right]$$

When $E_{ab} = E_{ad}$

$$R_n = \frac{R_x S}{Q} + \frac{qr}{P+q+r} \left[\frac{P}{Q} - \frac{P}{q} \right]$$

If $\frac{P}{Q} = \frac{P}{q}$ then $R_n = \frac{P \cdot S}{Q}$

> Formula used :- unknown resistance of kelvin's double bridge

$$R = \frac{PS}{Q} \text{ in ohms}$$

>>> PROCEDURE :-

- The galvanometer is energized and the power supply +5v is checked.
- A 'Galvanometer' is connected externally to the galvanometer.
- The unknown resistance 'R' is connected in the galvanometer.
- The value of $P/Q = P/q = 0.1$ ratio
- The value of S is adjusted for proper balance and the value of "S" is noted and "R" is calculated from the formula.
- Unknown resistance = $R = \frac{PS}{Q}$ in Ω .

Teacher's Signature: _____

>> Tabulation

S.No.	P	Q	S	Measured value value. $R = P S / Q$	Set value R_n
Unit	Ω	$K\Omega$	$K\Omega$	ohms	ohms
1	1	1	10	10	10
2	1	1	10	90	100

P, Q :- First set of ratio arm

P, Q :- Second set of ratio arm

R_n = unknown resistance

S : standard resistance

R : Resistance of connecting lead

C_r : Galvanometer

E : internal battery

>> Model Calculation

$$R = \frac{P \times S}{Q} = \frac{1000 \times 10}{1000} = 10 \text{ ohms}$$

>> Result :-

The unknown value of resistance is found out using Kelvin's bridge.

$$R = 10 \text{ ohms}$$

Experiment: - 3

>> Aim:

To Calibrate use give ammeter by using potentiometer

>> APPARATUS: - Potentiometer 10 wires, battery eliminator (0-5 V, 500 mA) battery eliminator (0-5 V, 2 A), Daniel cell, ar. dry cell, two way key and connecting wires.

>> THEORY: - The connecting are self-explanatory. In this circuit experiment the same current as simultaneously measured with the given instrument as potentiometer and a given ammeter. Hence the error in the given instrument as del. Let l_1 be the balancing length of potentiometer wire when emf 'E' of a Daniel cell in balanced it. then we have

$$E = \lambda l_1$$

where ' λ ' is the potential gradient along the potentiometer wire. $\therefore \lambda = \frac{E}{l_1}$ (1)

Let l_2 be the balancing length of potentiometer wire, where potential difference V_2 across resistance R bet. M and N in balanced on it. there we have $V_2 = \lambda l_2$ (2)

From (1) & (2) we have $V_2 = \sum n(I_2/I_1)$

$$i_2 = V_2 \dots (3)$$

Substituting value of V_2 from (3) in (2)

$$i_2 = \sum n \left(\frac{l_2}{l_1} \right) \dots (4)$$

here

i_2 : Current as measured by potentiometer when

$R = 1 \Omega$

i_1 : Current as measured by ammeter

E : emf of stand. cell / standard cell

l_1 : balancing length for standard cell

l_2 : balancing length of 1Ω resistance

$$\text{Error} = (i_1 - i_2)$$

If the reading of a given ammeter gives the same current in i_1 , the error is the reading of the instrument will be $(i_1 - i_2)$ with help of the battery eliminator B_2

Current can be viewed in the circuit and the

ammeter can be calibrated for its full range. A graph can then be prepared between reading and the corresponding

>> OBSERVATION:

emf of the standard cell = 1.08V

1.5 Beer dry cell

S.No	Balancing length of steel (cm)	Balancing length across wire (cm)	P.D across resistance $V_2 = E(d_2/d_1)$	Actual current (i ₂ = V ₂)	observed ammeter (i ₂ = V ₂)	Error (i ₁ - i ₂) Amp.
1	1000	34	0.098	0.098	0.1	0.002
2	1000	67	0.194	0.194	0.2	0.006
3	1000	100	0.290	0.290	0.3	0.10
4	1000	189.8	0.347	0.347	0.4	
5	1000	163.3	0.473	0.473	0.5	
6	1000	192.4	0.557	0.557	0.6	
7	1000	221.5	0.642	0.642	0.7	
8	1000	254	0.763	0.763	0.8	0.064
9	1000	288.8	0.837	0.837	0.9	0.063
10	1000	316.8	0.918	0.918	1.0	0.083
11	1000	345	1.000	1.000	1.1	0.100
12	1000	386	1.119	1.119	1.2	0.081
13	1000	407	1.180	1.180	1.3	0.120
14	1000	438	1.270	1.270	1.4	0.130
15	1000	472.5	1.370	1.370	1.5	0.130
16	1000	506.5	1.468	1.468	1.6	0.132
17	1000	543.9	1.577	1.577	1.7	0.123
18	1000	570.1	1.653	1.653	1.8	0.147
19	1000	601.3	1.743	1.743	1.9	0.157
20	1000	642	1.861	1.861	2.0	0.139
21	1000	673.5	1.953	2.053	2.1	1.47
22	1000	700	2.03	2.03	2.2	1.70
23	1000	737.4	2.138	2.138	2.3	0.17
24	1000	769.2	2.230	2.230	2.4	0.17

Teacher's Signature: _____

24	1000	827.5	2.399	2.399	2.4	0.201
25	1000	863.3	2.503	2.503	2.5	0.200
26	1000	898.4	2.605	2.604	2.6	0.200
27	1000	922.3	2.674	2.605	2.7	0.197
28	1000	958.2	2.650	2.677	2.8	0.198
29	1000	946.2	2.666	2.688	2.9	0.226
30	1000	958.2	2.775	2.774	3.0	0.272

→ Calculation:-

$$(1) \quad i_1 = 0.998 \text{ Amp}$$

$$(i_1 - i_2) = 0.002 \text{ Amp}$$

$$(2) \quad i_2 = 0.194 \text{ Amp}$$

$$(i_1 - i_2) = 0.006 \text{ Amp}$$

$$(3) \quad i_2 = 958.2$$

$$(i_1 - i_2) = 0.222$$

Experiment: 04

AIM:-

To measure low resistance by Compton Potentiometer.

APPARATUS:-

Compton potentiometer, New Tech type NTI 501, two battery eliminators, two rheostats, two one-way key, one galvanometer, one known resistance of comparatively higher value and given small resistance.

THEORY:-

Let I current is passing through known resistance R of comparatively higher value and small unknown resistance r . The balancing length corresponding to potential drop on R is l_1 .

$$\therefore IR = \phi l_1 \quad \text{--- (1)}$$

where G is potential gradient.

If balancing length corresponding to potential drop on $(R+x)$ resistance is l_2 .

$$\text{then } l(R+x) = G l_2 \quad \text{--- (2)}$$

Putting the (2) (1) equation

$$\frac{R+x}{R} = \frac{j_2}{j_1}$$

$$\text{or } 1 + \frac{x}{R} = \frac{j_2}{j_1}$$

$$\text{or } \frac{x}{R} = \frac{j_2 - j_1}{j_1}$$

$$\text{or } x = \frac{j_2 - j_1}{j_1} R \quad \text{--- (iii)}$$

Putting the values of j_1 , l_2 and R in the formula the unknown low resistance x is calculated.

PROCEDURE:

- (i) Complete the connections as shown in fig (1).
- (ii) Close the keys K_1 and K_2 put plug in 'A' gap of way.
- (iii) Note down the balancing length l_1 , Bal. potential drop of R .
- (iv) Mean value of small resistance x is calculated.
- (v) Calculate the value of unknown small resistance, using formula.

$$x = \frac{l_2 - l_1}{l_1} R$$

OBSERVATIONS:

Ser. No.	Balance length l_1 Bal. P.D. or R cm	Balancing length l_2 Bal. P.D.	$x = \frac{l_2 - l_1}{l_1} R$ (ohms)
1			
2			
3			
4			

CALCULATIONS:

Putting value of l_1, l_2 and R in the formula the value of unknown small resistance x is calculated in each set of observation. Then mean value of x is determined.

RESULT:

The value of given small resistance, as determined using Wheatstone potentiometer is _____ Ohm.

Experiment - 05

AIM:-

To measure the displacement using LVDT.




APPARATUS:-

- (1) LVDT Setup
- (2) Resistors - $4.7\text{K}\Omega$ - $3\ 10\text{K}\Omega$
- (3) Signal generator
- (4) Digital multi-meter.

THEORY:-

The differential transformer is a passive inductive transformer also known as linear variable Differential transformer (LVDT.) LVDT has a soft iron core which slides within the hollow transformer & therefore effects magnetic coupling between the primary and two secondaries. The displacement to be measured is applied at its arm attached to soft iron core. When core is normal position (null), equal voltage are induced in the two secondaries. The frequency of ac applied to the primary winding ranges from 50Hz to 20kHz .

>> CIRCUIT DAIGRAM

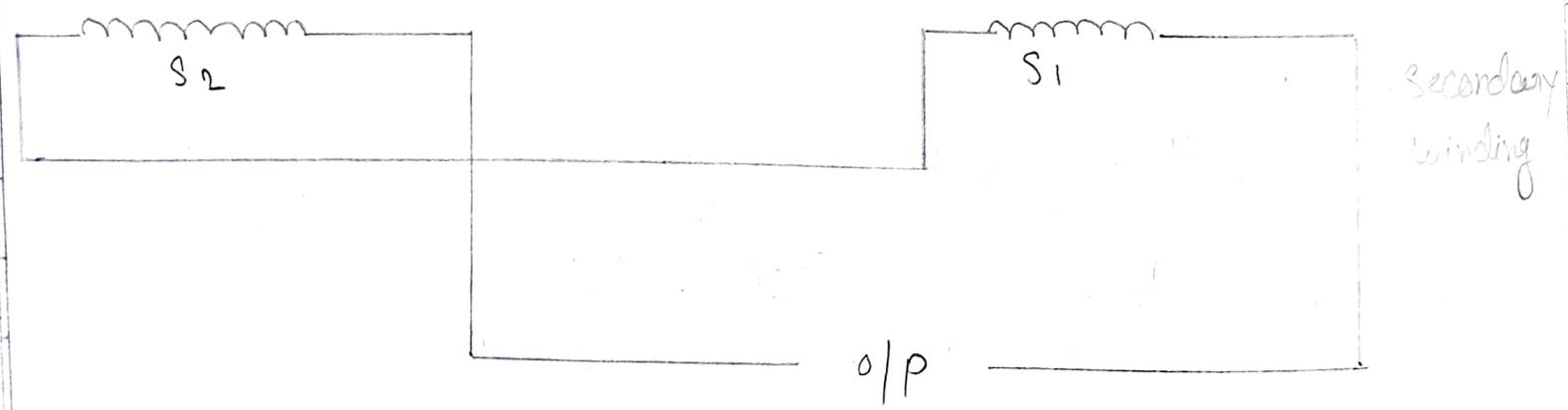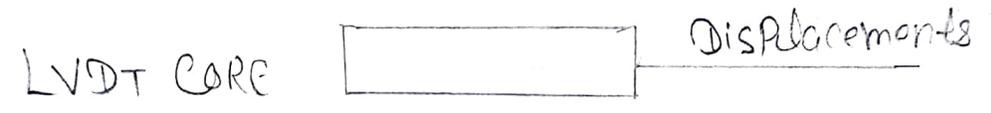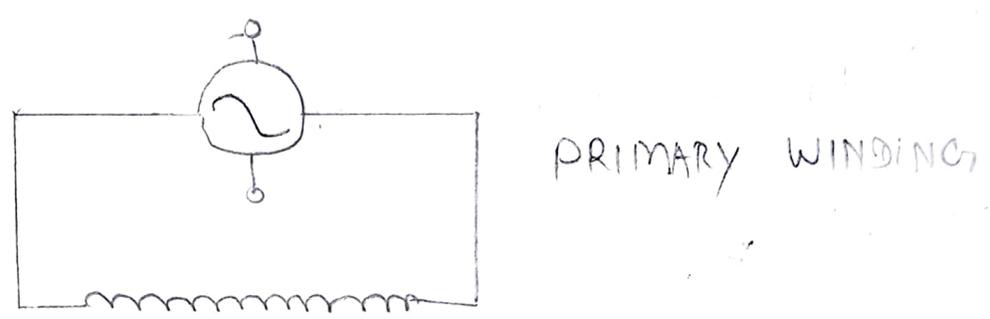

>> PROCEDURE:-

1. Connection are made as per circuit diagram
2. Initially setup core of LVDT at center.
3. Minimize the residual voltage with external balance CKT.
4. Change the core displacement. 1mm in one direction and observe the corresponding out put. voltage in DMM/CRO.
5. The core is moved forwards in other direction and take the reading for various displacements in steps.

>> A measurement:-

Residual voltage - 3.2 mv
 Minimum voltage - 0.7 mv

>> Color Code:-

Red & green / shield: Primary
 Yellow & green, centre black, Secondary

>> B Calibration:-

- (a) Initially set the core of an LVDT at a center position and observe the residual voltage at Null position.
- (b) Now Rotate the 10Kohm pot and observe the voltage in DMM such that it should be lowest reading which is approximately (0.6mv to 1.3mv)

S.NO	DISPLACEMENT (mm)	O/P VOLTAGE (mV)
1	0	0.7
2	1	9.1
3	2	17.9
4	3	26.3
5	4	35.4
6	5	44.6
7	6	33.7
8	7	63.3
9	8	72.8
10	9	81.8
11	10	91.0
12	1	8.3
13	2	16.9
14	3	23.5
15	4	34.4
16	5	42.8
17	6	52.4
18	7	62.48
19	8	71.5
20	9	80.5
21	10	90.2

» RESULT :-

Residual voltage = _____ mV

minimum voltage = _____ mV

Linear displacement range = _____ mm